



Bridge of Life
Education

SOC Design Verilog FSM Design


Jiin Lai

FSM Block Diagram


A sequential circuit which has

- External inputs
- Externally visible outputs
- Internal states

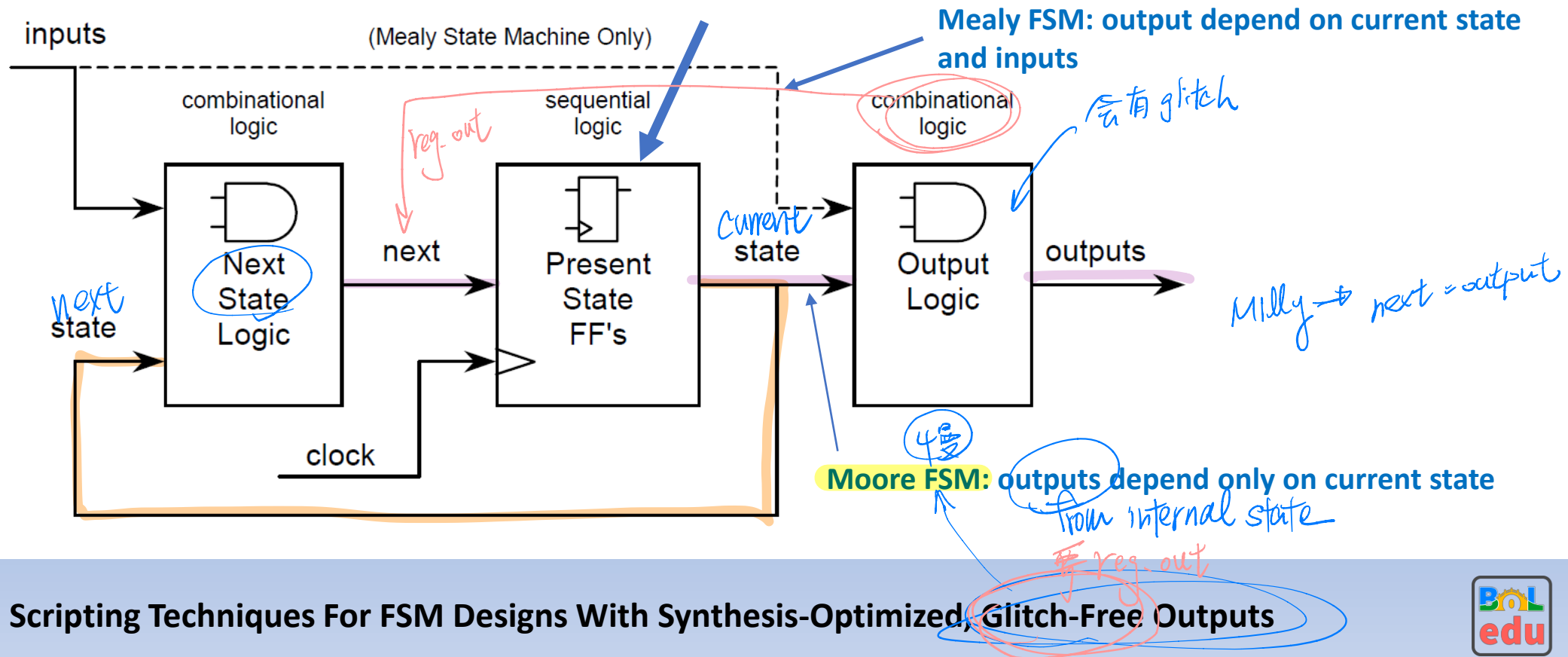- Store current state
- Load previously calculated next state
- # of states $\leq 2^{(\text{\# of FFs})}$



FSM Example

 

```
module fsm1a (ds, rd, go, ws, clk, rst_n);
    output ds, rd;
    input  go, ws;
    input  clk, rst_n;
```

```
    parameter [1:0] IDLE = 2'b00,
                  READ  = 2'b01,
                  DLY   = 2'b10,
                  DONE  = 2'b11;
```

State encoding

```
    reg [1:0] state, next;
```

```
    always @(posedge clk or negedge rst_n)
        if (!rst_n) state <= IDLE;
        else      state <= next;
```

```
    always @(state or go or ws) begin
```

```
        next = 2'bx;
        case (state)
            IDLE: if (go) next = READ;
                  else   next = IDLE;
```

```
            READ:      next = DLY;
```

```
            DLY:  if (ws) next = READ;
                  else   next = DONE;
```

```
            DONE:      next = IDLE;
```

```
        endcase
```

```
    end
```

```
    assign rd = (state==READ || state==DLY);
    assign ds = (state==DONE);
```


```
endmodule
```

State register,
sequential
always block

Next state,
combinational
always block

Continuous
assignment
outputs

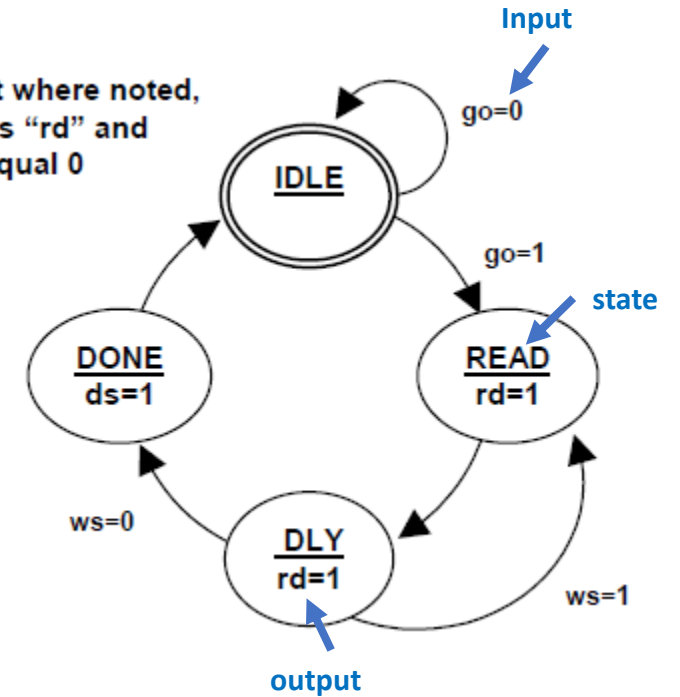Except where noted,
outputs "rd" and
"ds" equal 0



Merge output & next state logic in one always block

```
module fsm1 (ds, rd, go, ws, clk, rst_n);
    output ds, rd;
    input  go, ws;
    input  clk, rst_n;
    reg    ds, rd;

    parameter [1:0] IDLE = 2'b00,
                  READ  = 2'b01,
                  DLY   = 2'b10,
                  DONE  = 2'b11;

    reg [1:0] state, next;

    always @(posedge clk or negedge rst_n)
        if (!rst_n) state <= IDLE;
        else       state <= next;


    always @(state or go or ws) begin
        next = 2'bx;
        ds = 1'b0;
        rd = 1'b0; default
        case (state)
            IDLE: if (go)    next = READ;
                  else      next = IDLE;

            READ: begin      rd  = 1'b1;
                           next = DLY;
                  end

            DLY:  begin      rd  = 1'b1;
                           if (ws) next = READ;
                           else  next = DONE;
                  end

            DONE: begin      ds = 1'b1;
                           next = IDLE;
                  end

        endcase
    end
endmodule
```

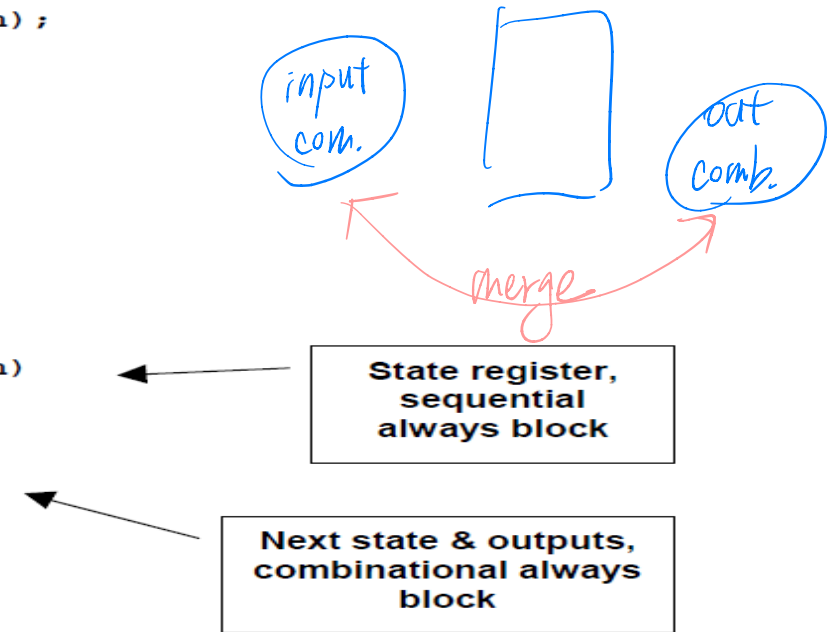


Problem with the two implementation

1. **Combinational** outputs can **glitch** between states.

```
assign rd = (state==READ || state==DLY);  
assign ds = (state==DONE);
```

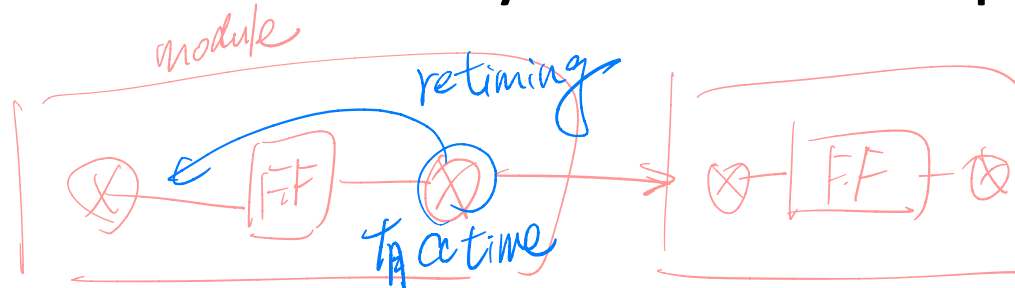2. Combinational outputs **consume part of the overall clock cycle** that would have been available to the block of logic that is driven by the FSM outputs.





★ Module Partition for Synthesis – Registered out

Registered out


- All output are registered
- All combinational logic is on the input-side or between registered stages
- Simplify the task of **constraining a design** for synthesis
- Better meet **timing** requirement

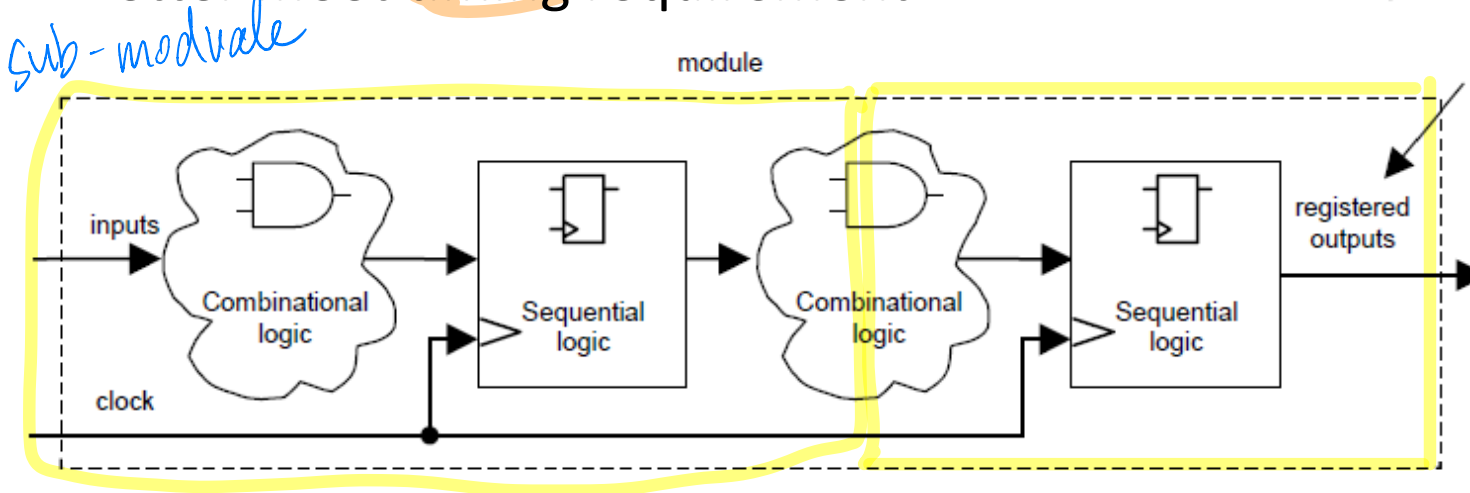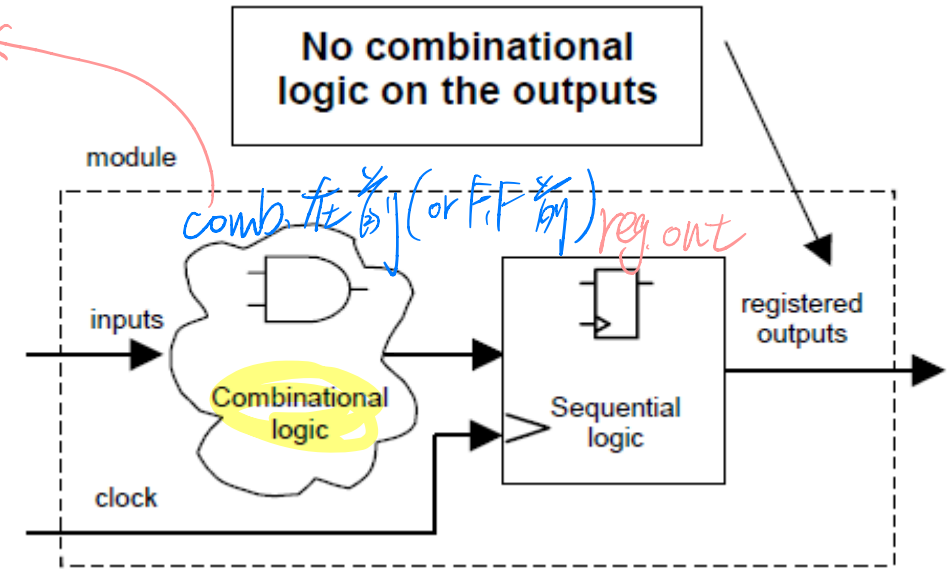① *constrain design easily*
② *better time*




Why not both registered in and registered out?

Generate and Registering “next output”

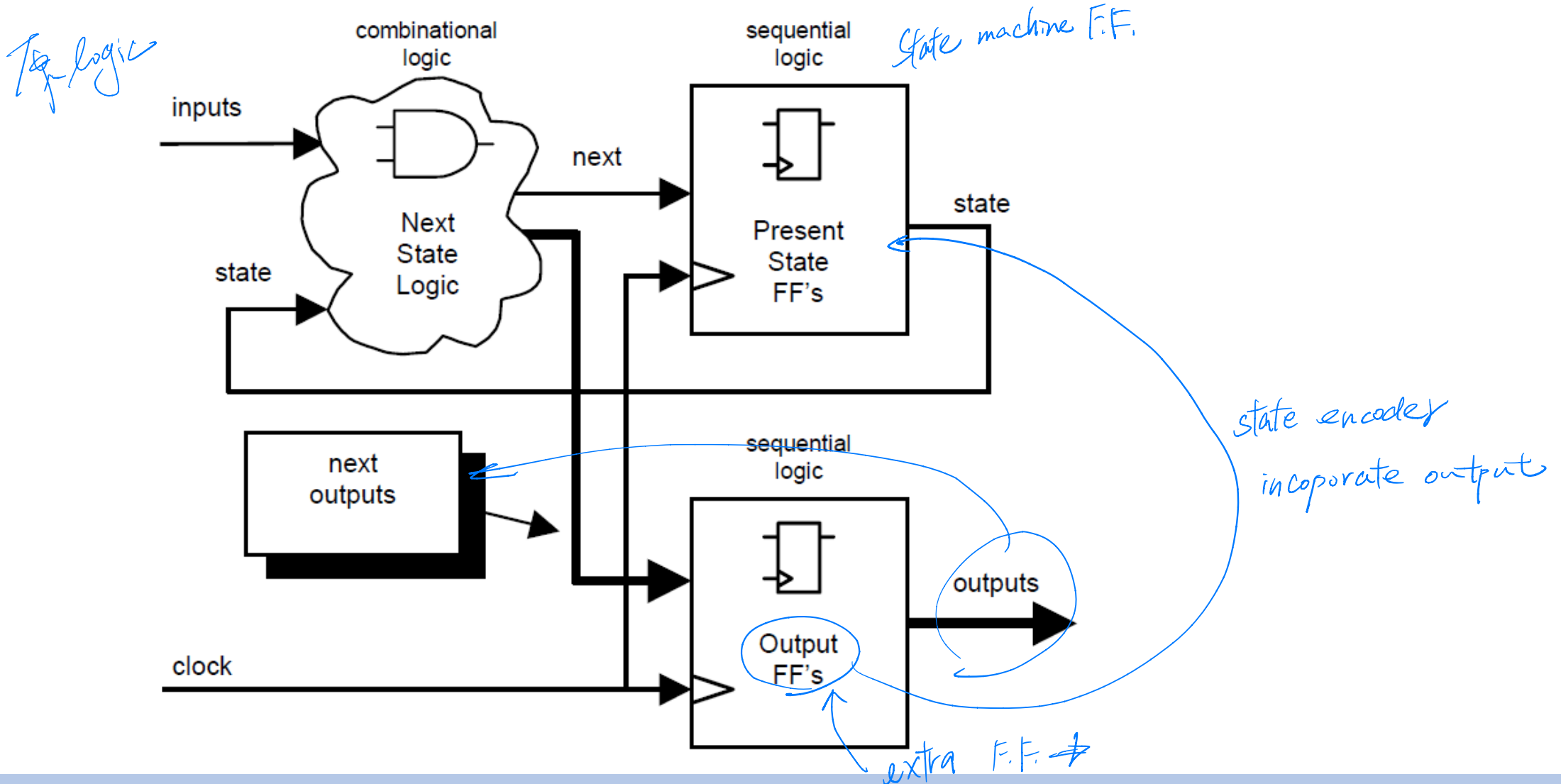

Output Encoded FSM

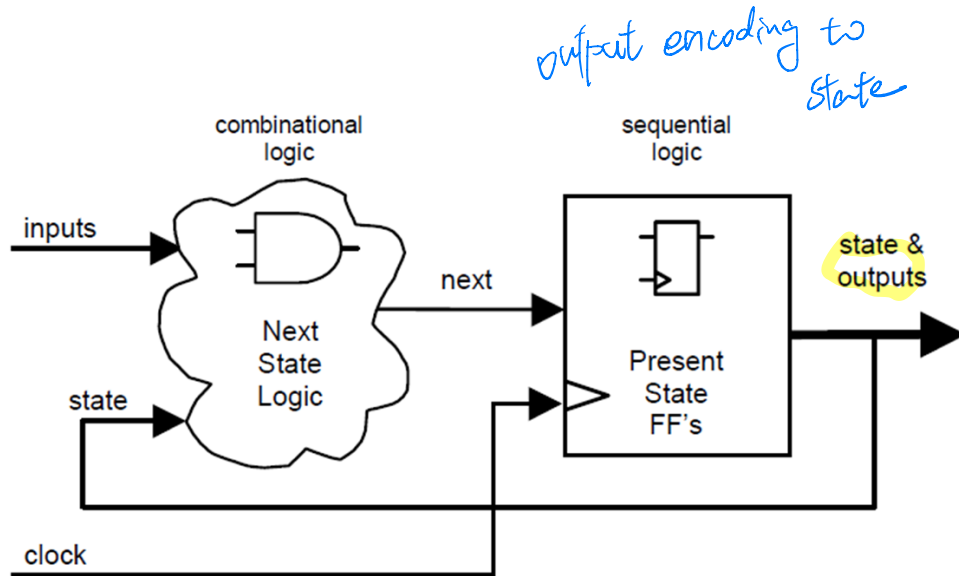select a state encoding that forces the outputs to be driven by individual state-register bits



```
module fsm1a_ff01 (ds, rd, go, ws, clk, rst_n);
    output ds, rd;
    input  go, ws;
    input  clk, rst_n;
```

```
// state bits = x0    ds rd
parameter [2:0] IDLE = 3'b0_00,
                READ  = 3'b0_01,
                DLY   = 3'b1_01,
                DONE  = 3'b0_10;
```

ds rd 1/2 output

State encoding

```
reg [2:0] state, next;
```

```
always @(posedge clk or negedge rst_n)
    if (!rst_n) state <= IDLE;
    else      state <= next;
```

State register,
sequential
always block



```
always @(state or go or ws) begin
    next = 3'bx;
    case (state)
        IDLE: if (go) next = READ;
              else   next = IDLE;
        READ:  next = DLY;
        DLY:   if (ws) next = READ;
              else   next = DONE;
        DONE:  next = IDLE;
    endcase
end
```

Next state,
combinational
always block

```
assign {ds,rd} = state[1:0];
endmodule
```

Outputs are
assigned directly
from the state-
register bits

Mealy Outputs

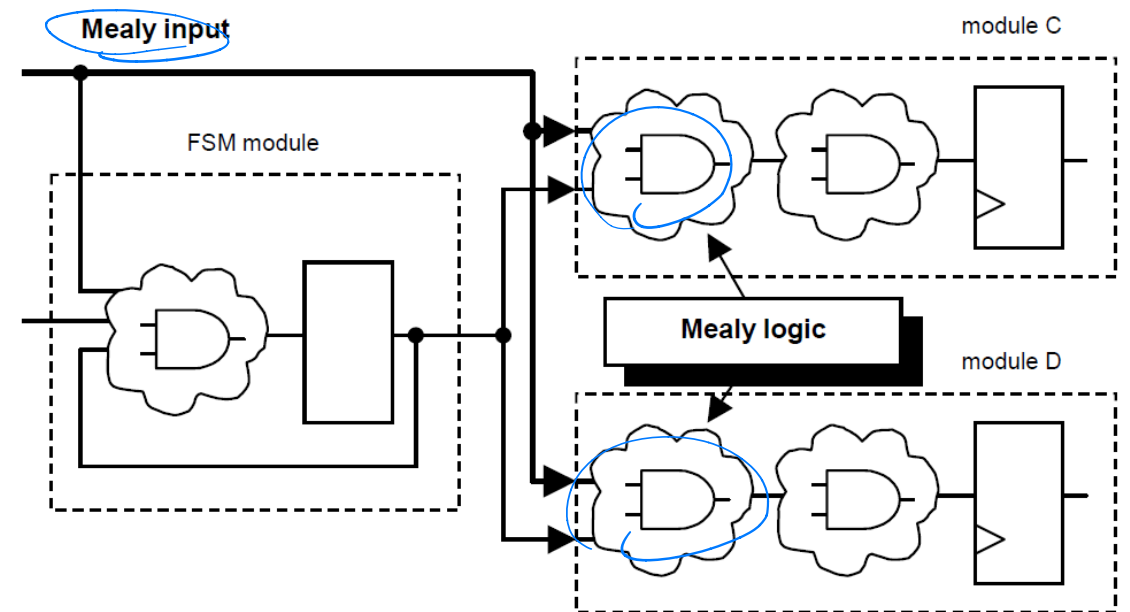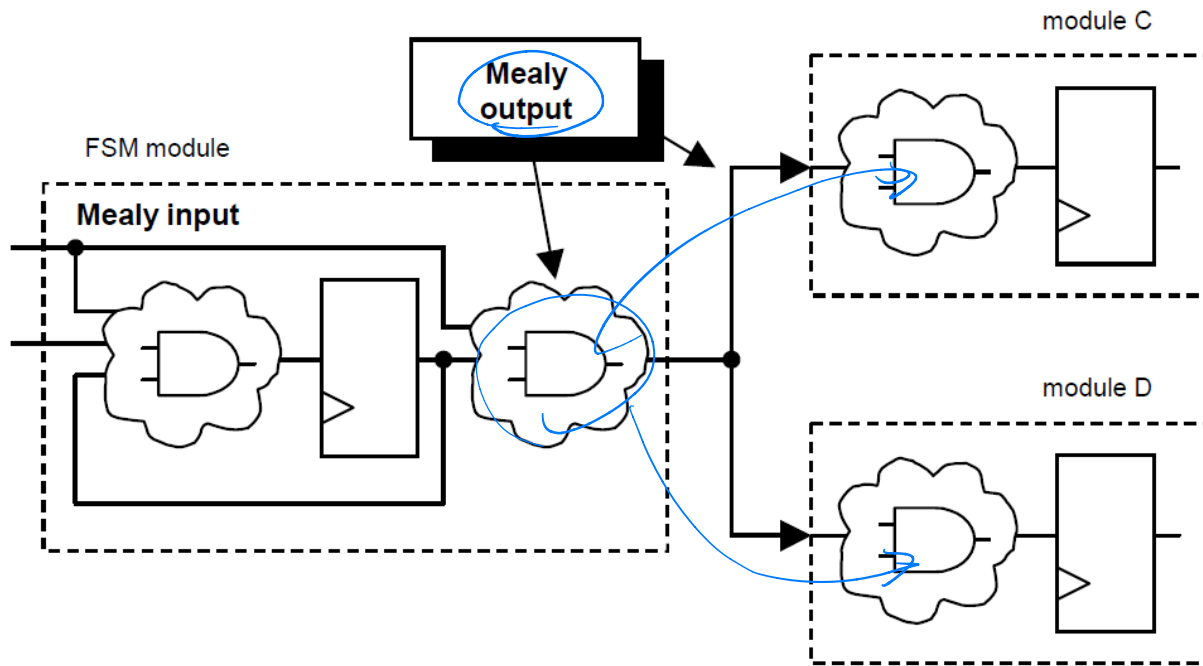


Edge Detector Implementation : Mealy & Moore FSM


Input: A bit stream that is received one bit at a time.

Output: Asserts its output to be true when the input bit stream changes from 0 to 1.


Mealy FSM

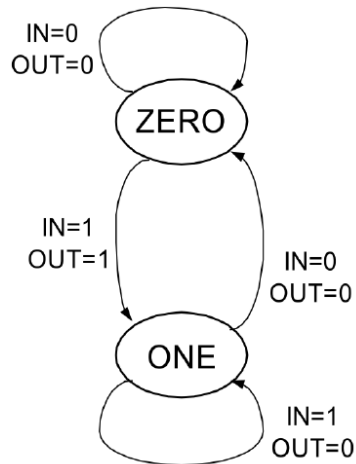

Moore FSM

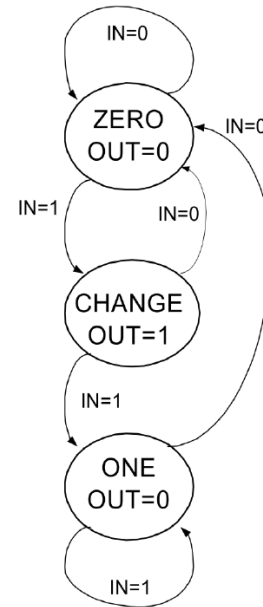

detect rising edge → gen. pulse

 


*pulse width
IN strict timing require*

FSM Comparison

Moore Machine

 - output function only of current state
- maybe more states (why?)
- synchronous outputs
 - Input glitches not send at output
 - one cycle “delay”
 - full cycle of stable output



Mealy Machine

- output function of both current & input
- maybe fewer states
- asynchronous outputs
 - if input glitches, so does output
 - output immediately available
 - output may not be stable long enough to be useful (below):

Hand-drawn diagram showing a glitch in the output of a Mealy Machine. A vertical arrow points down to the word "glitch".

Summary: FSM Design Process

- Specify circuit function
- Draw state transition diagram
- Write down symbolic state transition table
- Write down encoded state transition table (Encode State Machine)
- Derive logic equations
- Derive circuit diagram
- Register to hold state
- Combinational logic for next state and outputs